

Home-based Treatments

I MAKE NO CLAIMS THAT ANYTHING HERE CAN CURE ANY FORM OF ILLNESS. HOWEVER, THE VERY SIMPLE “COLLOIDAL SILVER” WHICH IS JUST VERY TINY CHARGED PARTICLES OF PURE SILVER SUSPENDED IN DISTILLED WATER HAS BEEN VERY HELPFUL IN THE PAST:


COLLOIDAL SILVER HAS CURED MANY ‘TERMINALLY ILL’ CANCER PATIENTS OF CANCER, IT HAS ELIMINATED SWINE ‘FLU, LYME’S DISEASE, TYPHUS, MALARIA, CHOLERA AND AMOEBIC DYSENTERY. IT CONVERTS CANCER CELLS BACK INTO HEALTHY CELLS AND IT HAS BEEN SUCCESSFUL IN DEALING WITH OSTEOMYELITIS, DIABETES AND TISSUE DAMAGE. IT HAS NO SIDE EFFECTS AND IS EASY TO MAKE.

THE FIRST REQUIREMENT IS DISTILLED WATER AND A CHEAP ‘PARTS PER MILLION’ METER CAN CONFIRM THE QUALITY OF THE WATER :



THE SECOND REQUIREMENT IS 99.99% PURE SILVER WIRE, A BATTERY, A GLASS CONTAINER, A NON-METAL STIRRER AND TWO CONNECTING WIRES.


THE ARRANGEMENT IS SIMPLE :

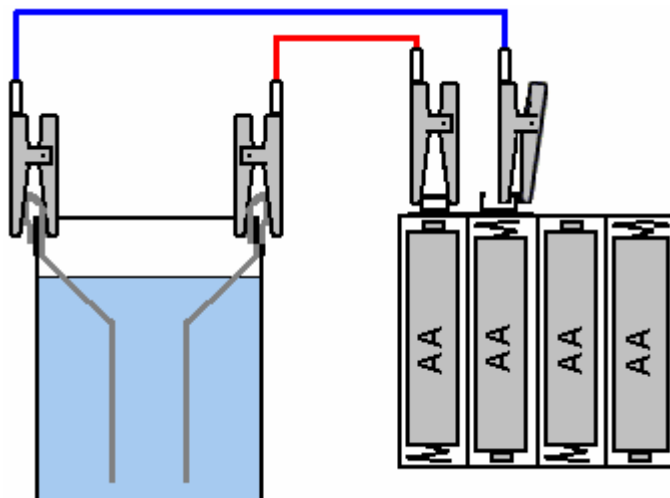

THE WATER IS PLACED IN A GLASS CONTAINER AND TWO PIECES OF SILVER WIRE ARE CLIPPED TO IT SO THAT THEY FORM ELECTRODES WHICH ARE PERHAPS HALF AN INCH

(12 mm) APART. THE BATTERY IS CLIPPED TO THE ELECTRODE WIRES AND THE WATER IS STIRRED WHILE THE COLLOIDAL SILVER IS BEING CREATED.

THE BATTERY CAN BE ANY TYPE :

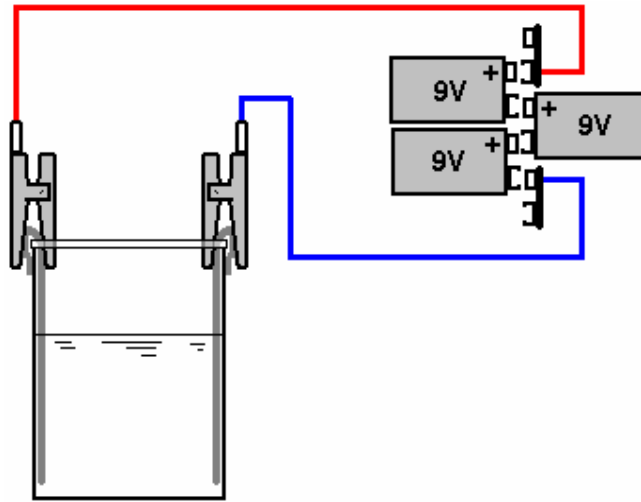



IT TAKES ONLY A FEW MINUTES TO MAKE THE COLLOIDAL SILVER AND THE WATER SHOULD BE STIRRED ALL THE TIME. THE TARGET IS 10 PARTS PER MILLION AND THE PPM METER SHOWS YOU WHEN YOU HAVE REACHED THAT CONCENTRATION. THE ELECTRODE CONNECTED TO THE BATTERY MINUS TERMINAL WILL BECOME COVERED WITH A BLACK DEPOSIT WHICH MAY NEED TO BE WIPED OFF WITH A FRESH TISSUE DURING THE PREPARATION. STORE THE SILVER WIRE AWAY FROM THE AIR SO THAT IT DOES NOT OXIDISE.

PLACING ABOUT 10 cc OF COLLOIDAL SILVER UNDER THE TONGUE FOR A PERIOD OF A MINUTE OR SO, SEVERAL TIMES PER DAY IS EFFECTIVE AS THE SILVER PARTICLES ENTER THE BLOODSTREAM AND TREAT EVERYWHERE IN THE BODY AT THE SAME TIME.


USING A NEBULISER IS ALSO EFFECTIVE WHEN TREATING A LUNG PROBLEM :



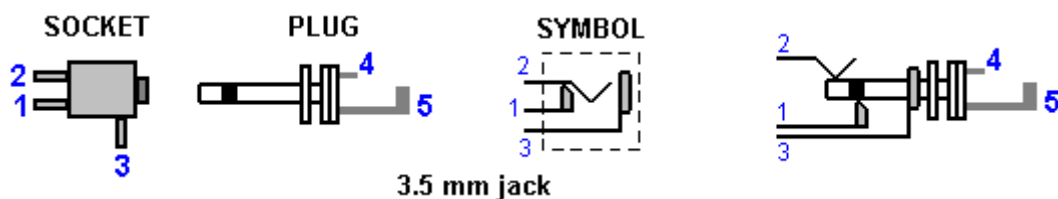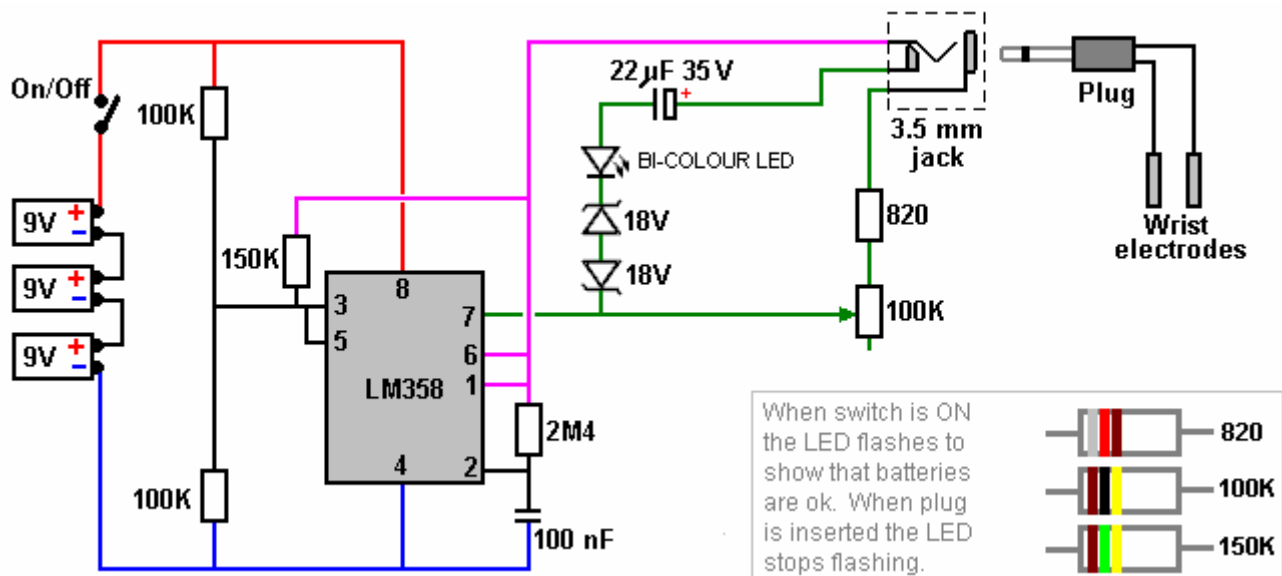ANOTHER HIGHLY THOUGHT OF TREATMENT IS THE BOB BECK PROTOCOL WHERE HE SUPPLEMENTS TAKING COLLOIDAL SILVER WITH A LOW FREQUENCY ELECTRONIC PULSE APPLIED TO EACH WRIST. HIS DOCUMENT IS : <http://www.free-energy-info.com/Beck.pdf> AND HIS EQUIPMENT CAN BE CONSTRUCTED QUITE EASILY. HERE IS HIS CIRCUIT :




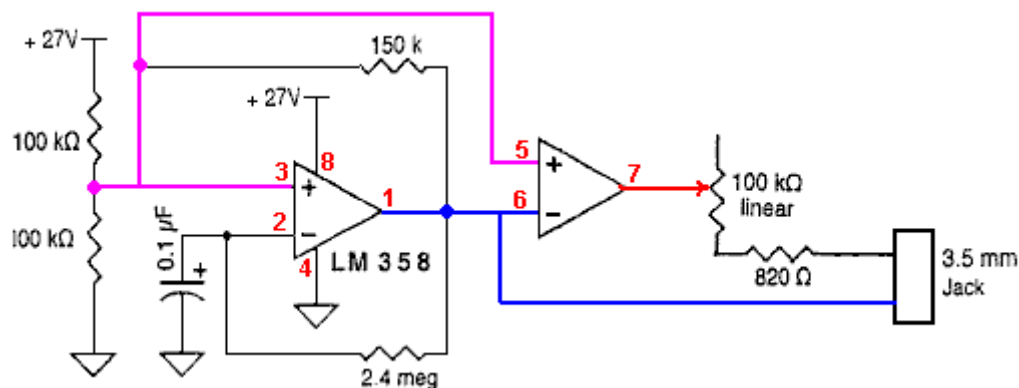IT MAY BE EASIER TO UNDERSTAND THE CIRCUIT IF IT IS SHOWN LIKE THIS :



THE FIRST OPERATIONAL AMPLIFIER INSIDE THE LM358 CHIP ACTS AS A SLOW OSCILLATOR, SWITCHING ABOUT FOUR TIMES PER SECOND. THE SECOND OPERATIONAL AMPLIFIER PASSES THAT SIGNAL TO THE OUTPUT SOCKET THROUGH THE VARIABLE RESISTOR AND ITS MINIMUM-SETTING 820 OHM RESISTOR.

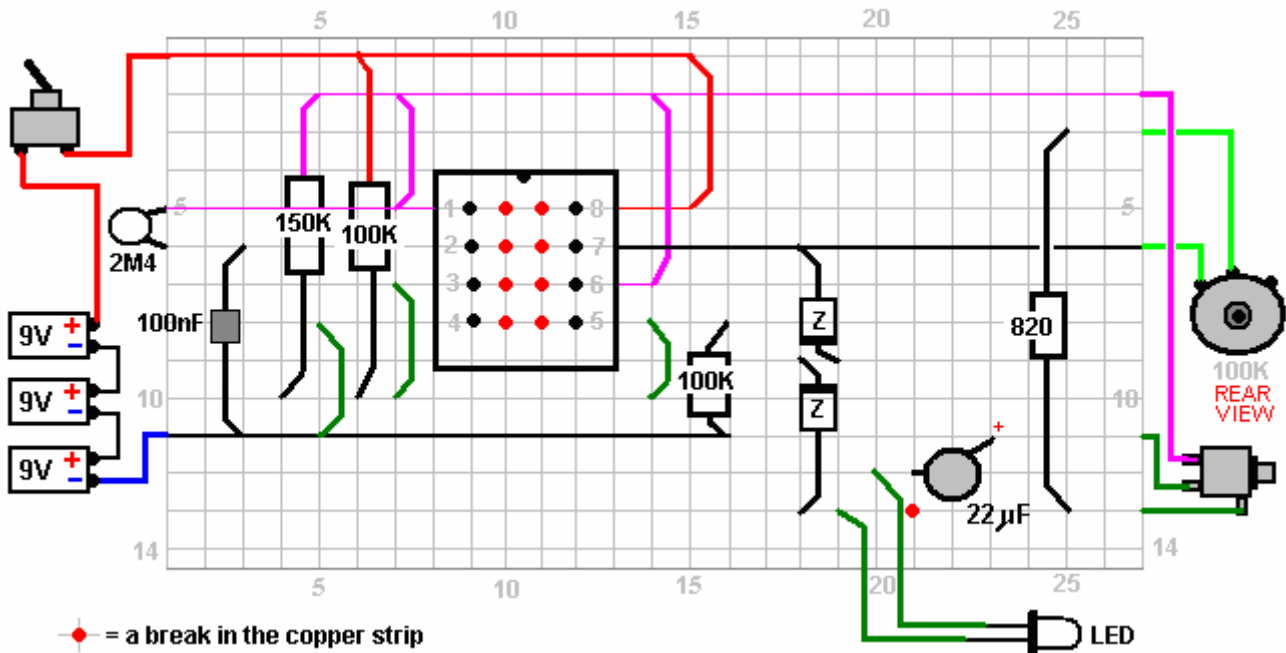A PHYSICAL CONSTRUCTION LAYOUT MIGHT BE :




THIS DESIGN IS VERY NEAT AND CAN BE HOUSED IN A PLASTIC BOX 100 x 70 x 40 mm IN SIZE, INCLUDING THE BATTERIES, VARIABLE RESISTOR, LED AND On/Off SWITCH. IT GENERATES A SIGNAL WHICH IS FIFTY VOLTS PEAK TO PEAK AND YOU NEED TO ADJUST THE VARIABLE RESISTOR SO THAT YOU CAN FEEL THE PULSES BUT THEY DO NOT HURT.

BROAD ELASTIC STRIP CAN BE USED IN A LOOP TO HOLD THE UNIT TO YOUR FOREARM AND TWO OTHER LOOPS TO HOLD EACH ELECTRODE TO EACH WRIST. TREATMENT IN TWO HOUR LONG SESSIONS IS RECOMMENDED.



AROUND 1920, GEORGE LAKOVSKY PRODUCED A VERY EFFECTIVE TREATMENT METHOD. AN AMERICAN DEVELOPER HAS KINDLY SHARED THE METHOD WHICH HE USED TO REPLICATE THIS EQUIPMENT :

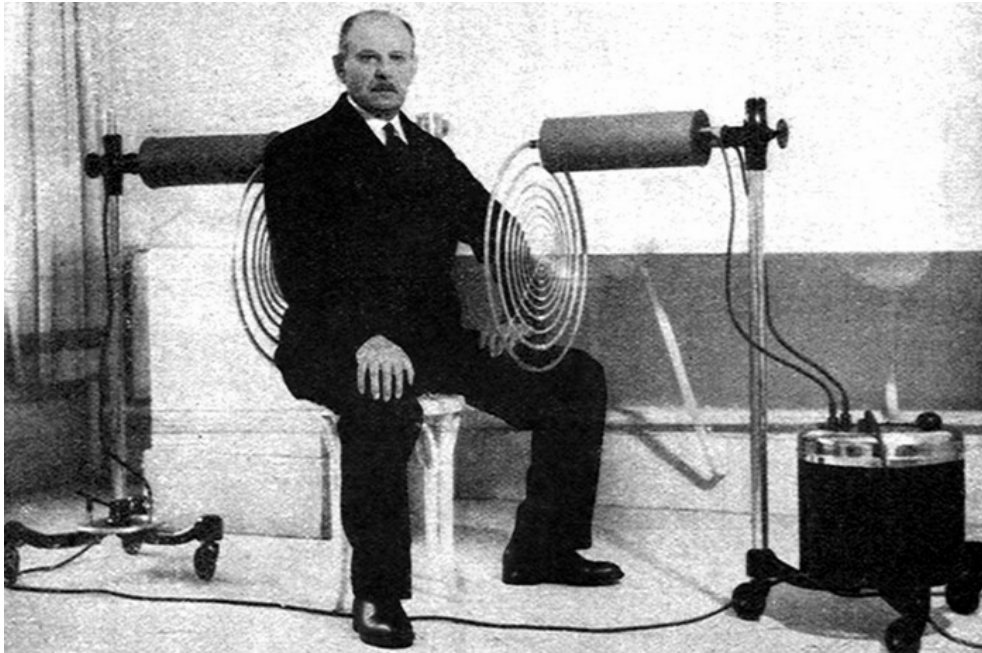THE IDEA IS TO ARRANGE TWO AERIALS TO TRANSMIT HEALING FREQUENCIES TO THE PATIENT :




THE FREQUENCIES OF THE WAVES TRANSMITTED BETWEEN THE AERIALS IS CONTROLLED BY THE LENGTHS OF THE AERIAL TUBES :




THE TWO AERIALS ARE CONSTRUED FROM FLEXIBLE COPPER PIPE AVAILABLE FROM CHINA.

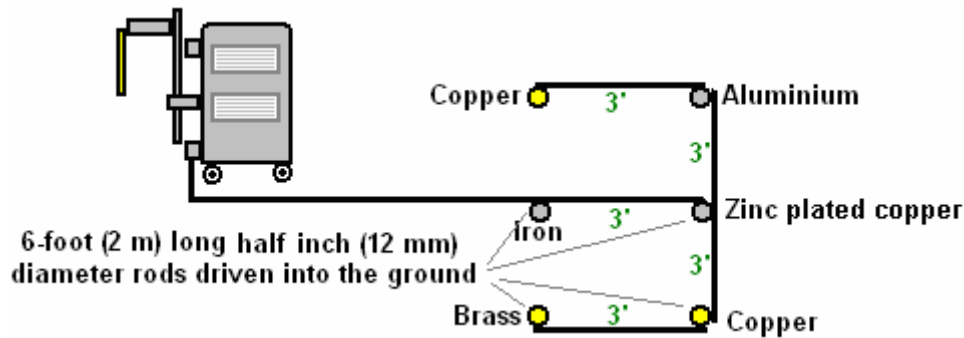
IT IS IMPORTANT THAT A SYSTEM OF THIS TYPE HAS A VERY EFFECTIVE EARTH CONNECTION WHICH IS NOT PART OF THE MAINS SUPPLY SYSTEM. IN THIS CASE, SEVERAL DIFFERENT METALS ARE USED IN THE EARTHING :



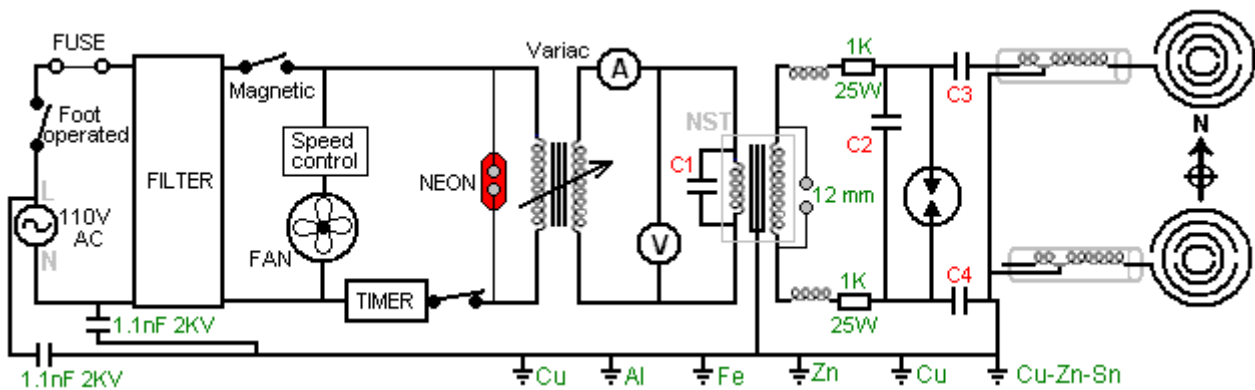THE CIRCUIT USED LOOKS COMPLICATED BUT IT REALLY ISN'T AND IT IS EASIER TO UNDERSTAND WHEN BROKEN DOWN INTO PARTS :




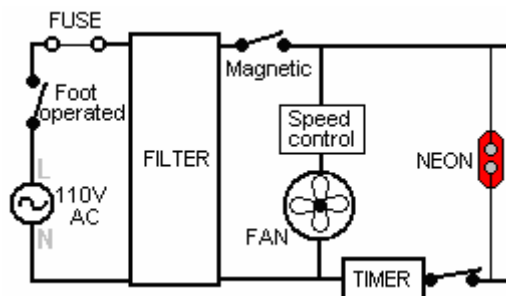THE FIRST PART OF THIS CIRCUIT IS JUST THE POWER SUPPLY FROM THE MAINS ALONG WITH PROTECTION FEATURES :




THERE IS A FOOT-OPERATED SWITCH WHICH ALLOWS THE PATIENT TO SWITCH THE SYSTEM OFF INSTANTLY AT ANY TIME. THE FUSE PROTECTS AGAINST A SHORT-CIRCUIT ANYWHERE IN THE EQUIPMENT. THE FILTER CLEANS UP THE POWER SUPPLY AND THE MAGNETIC SWITCH IS MOUNTED ON THE OPERATOR'S CONSOLE SO THAT THE OPERATOR CAN SWITCH OFF THE EQUIPMENT INSTANTLY (ALTHOUGH I HAVE NEVER HEARD OF THAT BEING NEEDED).

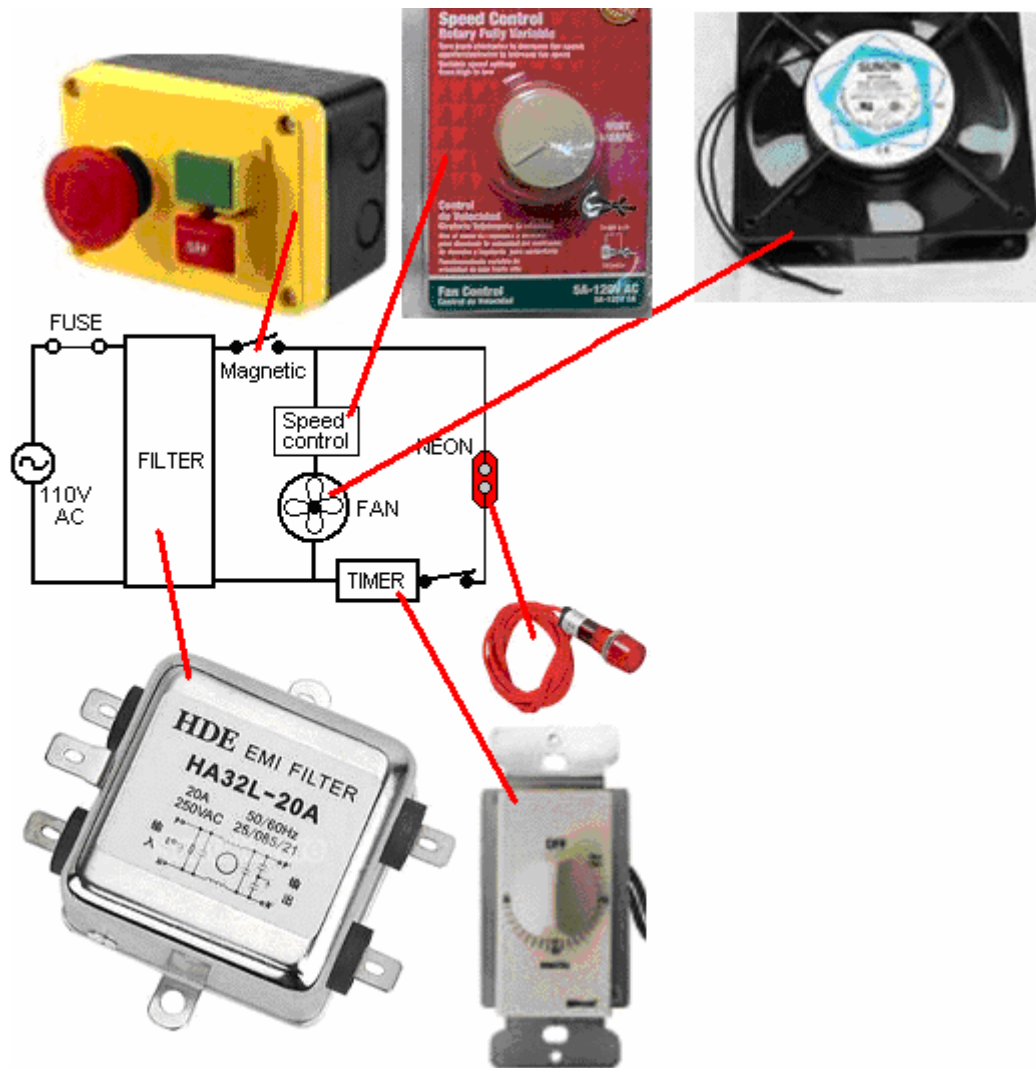THE FAN AND IT'S SPEED CONTROLLER ARE ONLY FOR KEEPING THE EQUIPMENT COOL AND THE TIMER ALLOWS A TREATMENT OF A FIXED PERIOD OF TIME TO BE SET (TYPICALLY 15 MINUTES). FINALLY, THE NEON BULB SHOWS THAT EVERYTHING IS WORKING UP TO THAT POINT. ALL THIS IS COMMERCIALY AVAILABLE AS CAN BE SEEN HERE :




THE WORKING PART OF THE CIRCUIT IS :

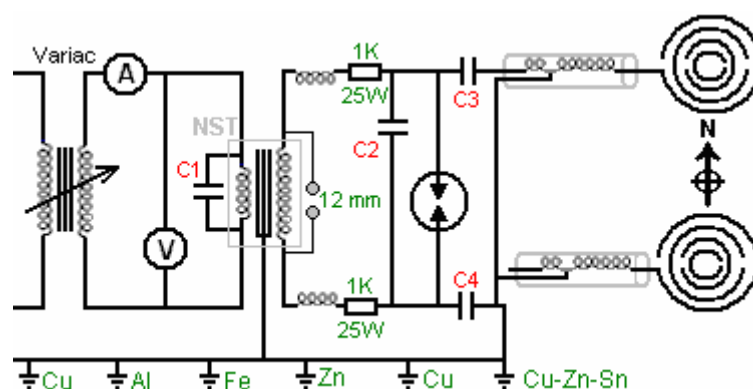

THE FIRST ITEM IS A VARIAC WHICH IS A VARIABLE VOLTAGE TRANSFORMER AND THAT ALLOWS THE VOLTAGE APPLIED TO THE REST OF THE CIRCUIT TO BE SET BY THE OPERATOR. THE CURRENT IS SHOWN ON THE AMMEYER "A" AND THE VOLTAGE FED TO THE REST OF THE CIRCUIT IS DISPLAYED ON THE VOLTMETER "V".

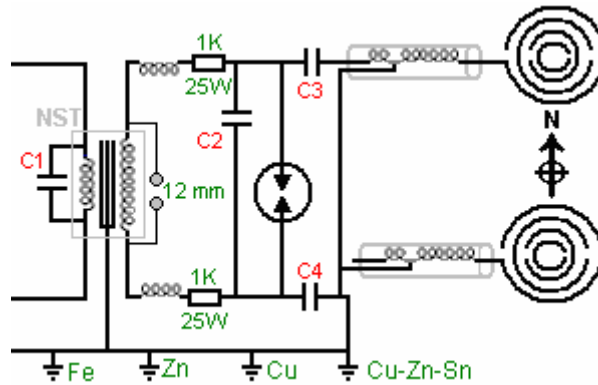THIS MEANS THAT THE OPERATIONAL PART OF THE CIRCUIT IS ONLY FOURTEEN COMPONENTS :



THE “NST” IS A NEON SIGN TRANSFORMER AND IT STEPS THE VOLTAGE UP TO THOUSANDS OF VOLTS, SO THAT THERE IS A HIGH VALUE ON THE CAPACITOR “C2” WHEN IT PASSES THROUGH THE TWO CHOKES AND TWO RESISTORS. THE 12 mm SPARK GAP ACROSS THE SECONDARY WINDING IS A SAFETY FEATURE GUARDING AGAINST THE REMAINDER OF THE CIRCUIT BECOMING DISCONNECTED.

THE HIGH VOLTAGE ON “C2” CAUSES THE SPARK GAP TO FIRE AND THAT FEEDS A WHOLE SERIES OF FREQUENCIES TO THE TWO AERIALS. YOU WILL NOTICE THE RECOMMENDED MAGNETIC ORIENTATION WHERE THE TWO AERIALS ARE ON A NORTH – SOUTH LINE WITH THE TRANSMITTER AERIAL ON THE NORTH SIDE.

FOR A DESIGN OF THIS TYPE, THE PHYSICAL CONSTRUCTION IS A MAJOR FACTOR, AND THE MOST IMPORTANT PART IS THE AERIALS. THESE ARE VERY CAREFULLY DIMENSIONED :

- Ring 1: Diam 500 mm, width 14.5 mm, depth 8 mm, copper diameter 14 mm, buy 144”
- Ring 2: Diam 400 mm, width 12.3 mm, depth 7 mm, copper diameter 12 mm, buy 120”
- Ring 3: Diam 320 mm, width 10.3 mm, depth 6 mm, copper diameter 10 mm, buy 96”
- Ring 4: Diam 275 mm, width 8.2 mm, depth 5 mm, copper diameter 8 mm, buy 72”
- Ring 5: Diam 225 mm, width 6.2 mm, depth 4 mm, copper diameter 6 mm, buy 115”
- Ring 6: Diam 184 mm, width 6.2 mm, depth 4 mm, copper diameter 6 mm.
- Ring 7: Diam 143 mm, width 6.2 mm, depth 4 mm, copper diameter 6 mm.
- Ring 8: Diam 112 mm, width 6.2 mm, depth 4 mm, copper diameter 6 mm.
- Ring 9: Diam 81 mm, width 6.2 mm, depth 4 mm, copper diameter 6 mm.
- Ring 10: Diam 51 mm, width 3.1 mm, depth 3 mm, copper diameter 3 mm. buy 36”
- Ring 11: Diam 30 mm, width 3.1 mm, depth 3 mm, copper diameter 3 mm.
- Ring 12: Diam 14 mm, width 3.1 mm, depth 3 mm, copper diameter 3 mm.



THESE DIMENSIONS ARE TO THE CENTRELINE OF EACH COPPER RING AERIAL.






EACH CIRCLE OF COPPER PIPE RADIATES ITS OWN SPECIFIC FREQUENCY ACROSS THE SPACE BETWEEN THE TWO COMPLETED AERIALS, SO THE WAVEFORM USED TO BENEFIT THE PATIENT IS A COMPOSITE OF TWELVE DIFFERENT FREQUENCIES. THE FULL DETAILS FOR CONSTRUCTION AND USE ARE IN <http://www.free-energy-info.com/PJKbook.pdf> WHICH IS A FREE DOWNLOAD.

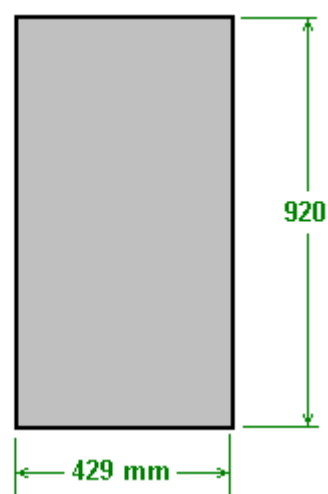
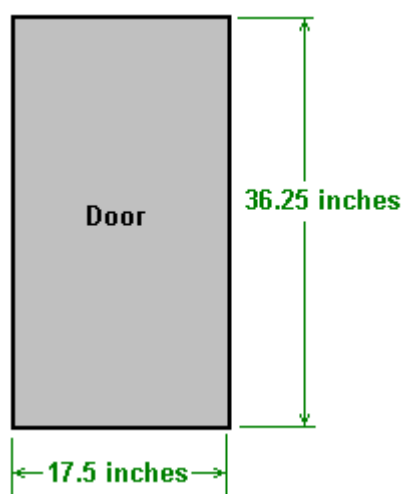
THE CONSTRUCTIONAL DETAILS ARE STRAIGHTFORWARD, RANGING FROM THE CASE :




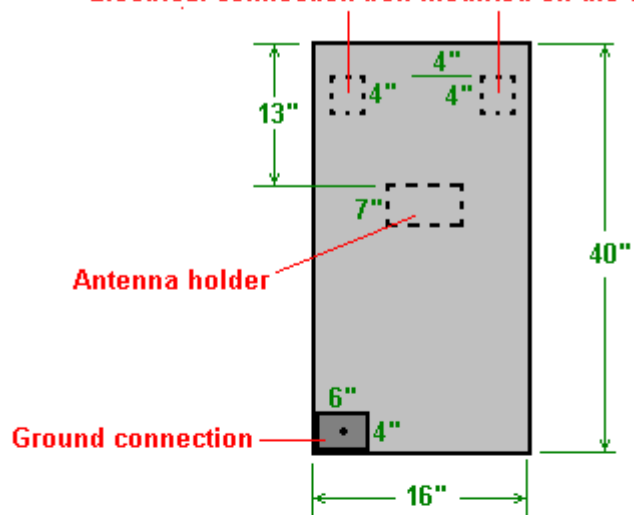
Electrical connection box mounted on the outside




Front panel (facing the aerials)

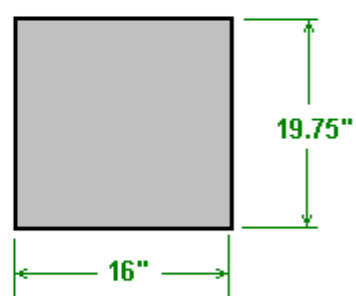
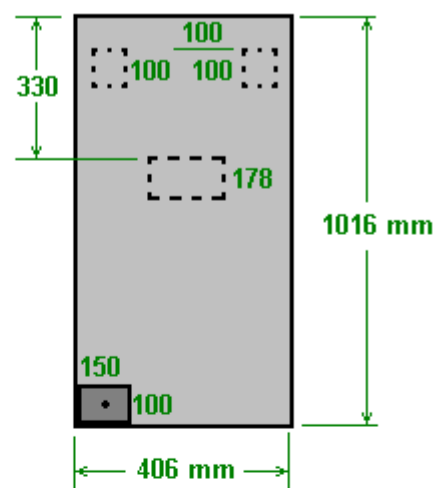






Base panel

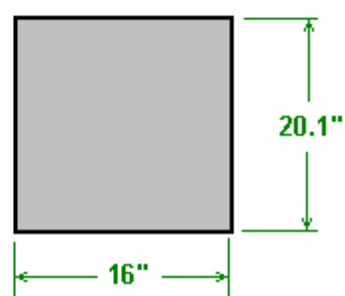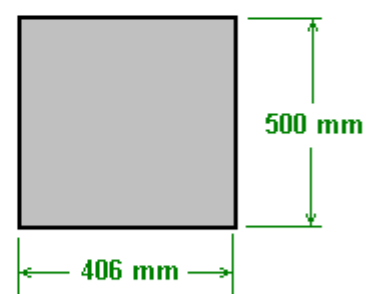


Top panel

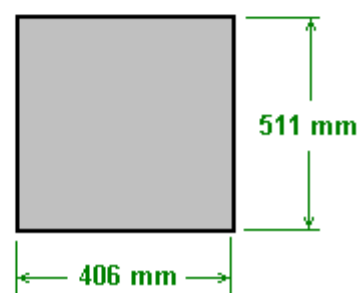

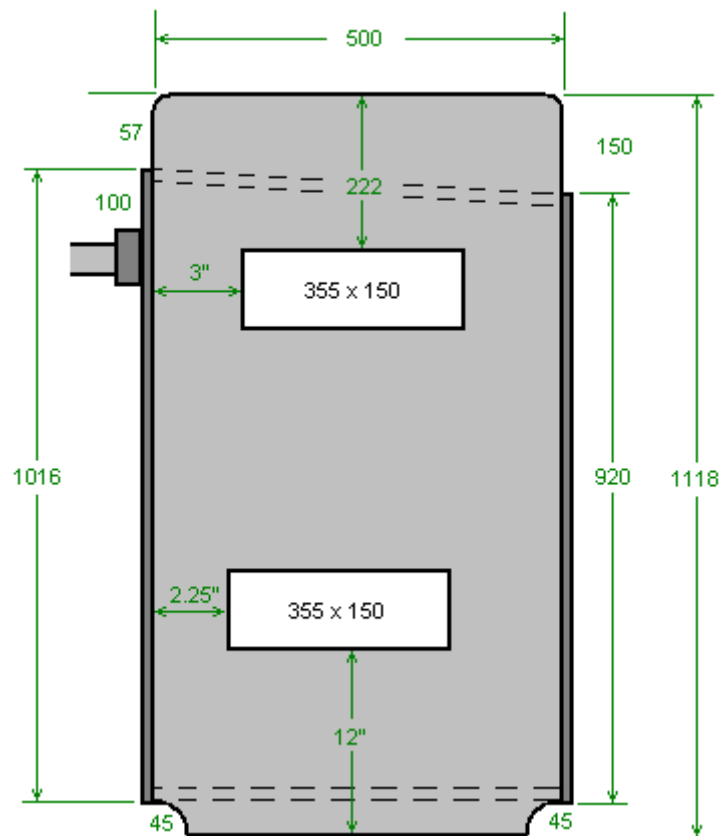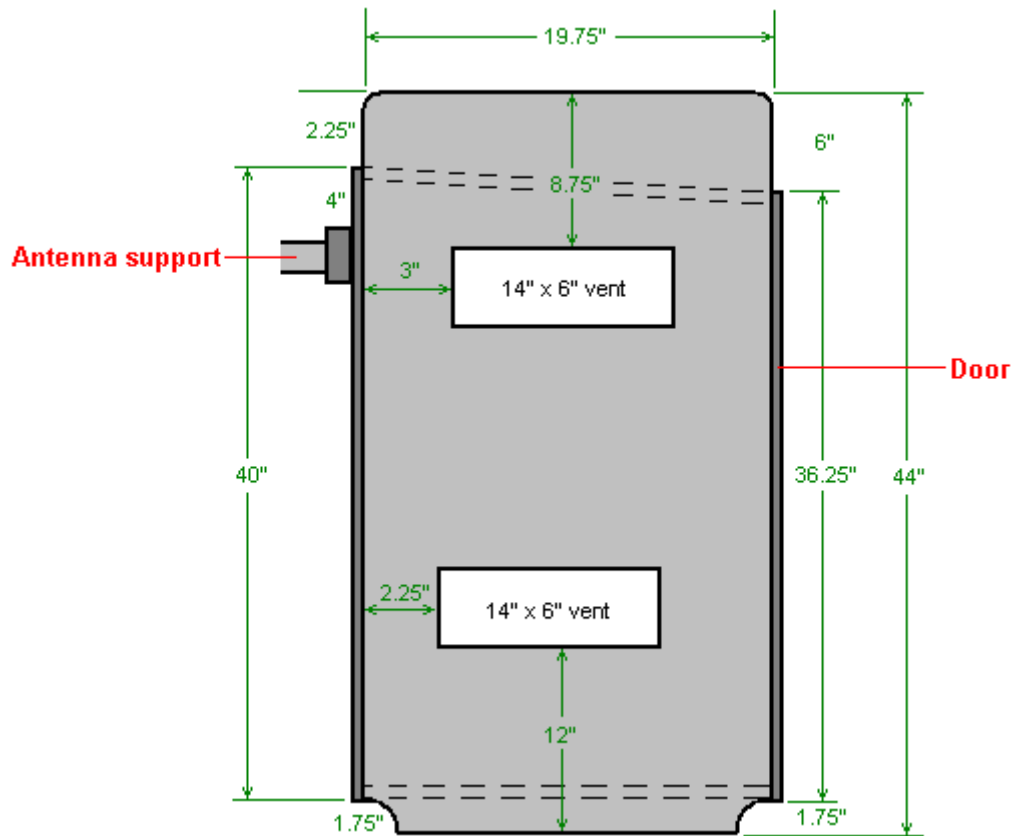


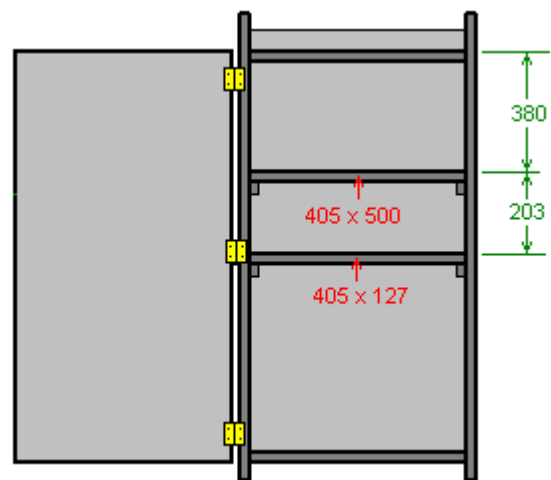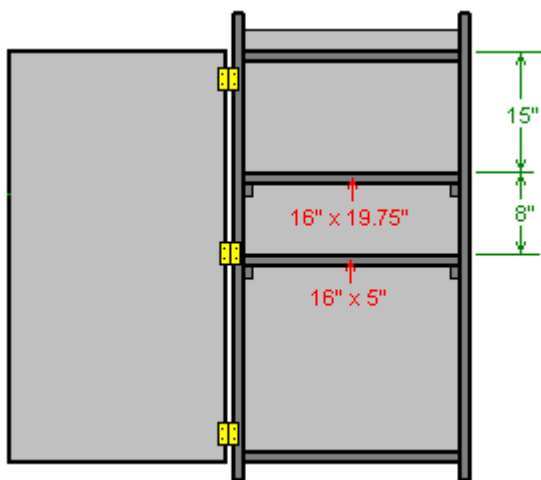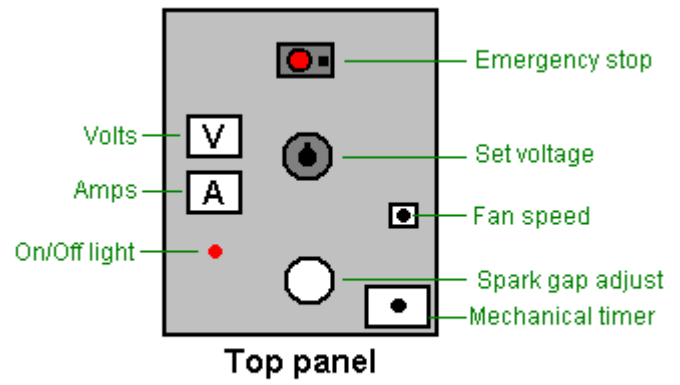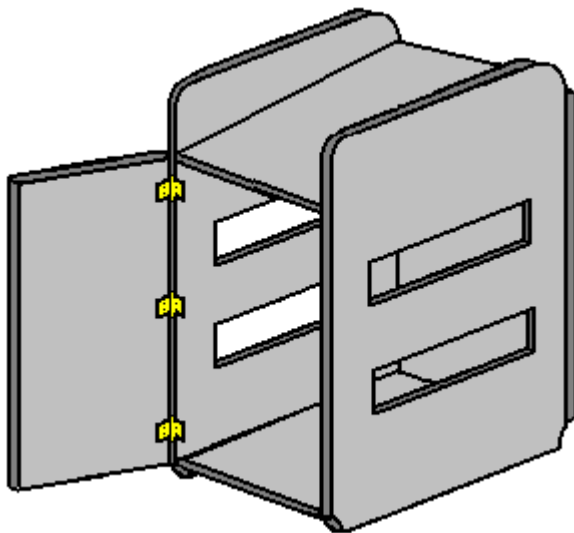

TO THE PHYSICAL WIRING :

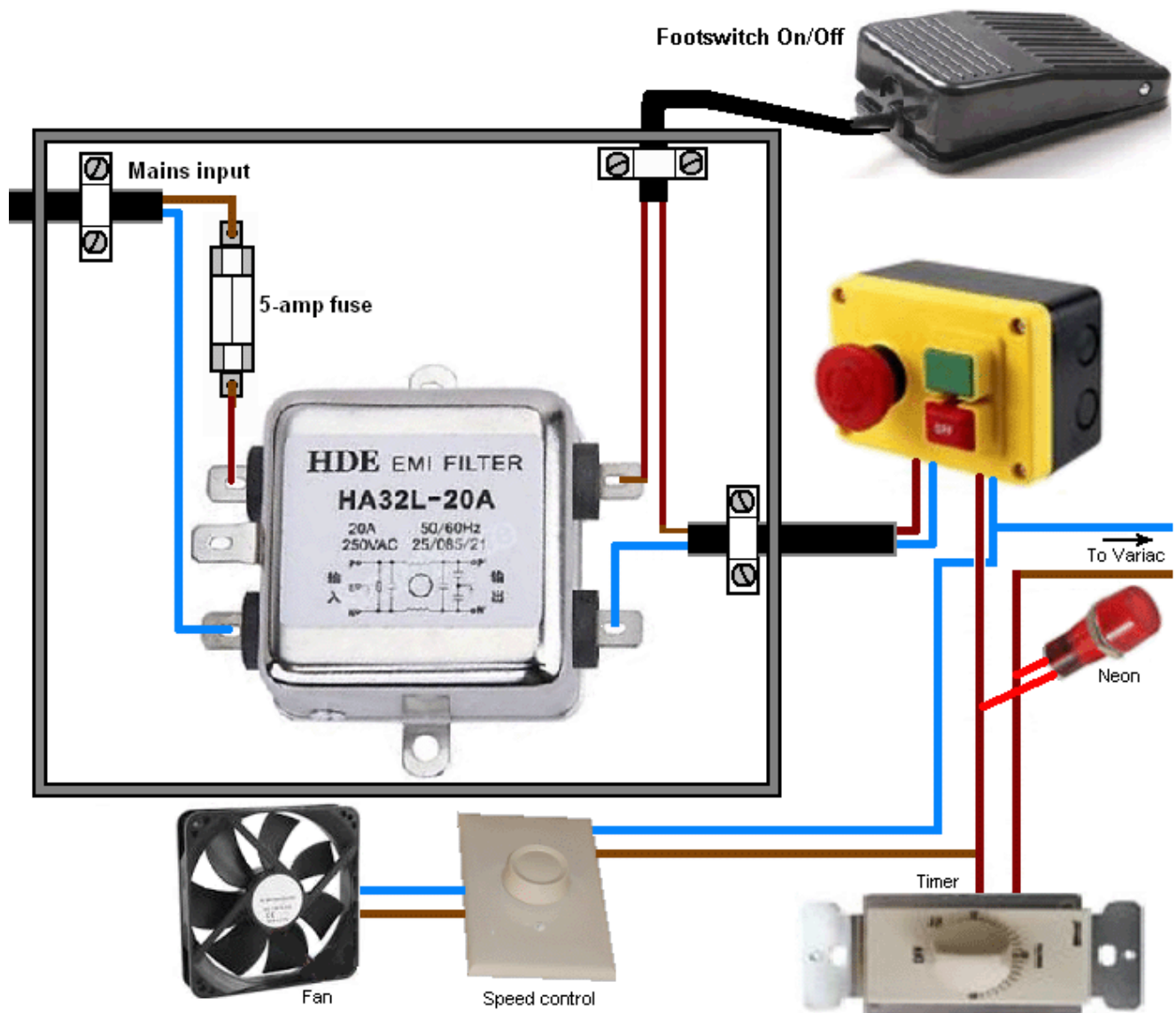

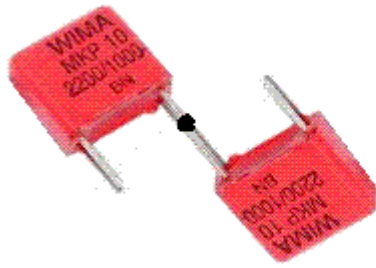VARIABLE AC
TRANSFORMER # 116CU
AC OUTPUT VARIAC 0-140VAC
60HZ. @ 10AMPS 1.4KVA
(351375018893)



10pcs - WIMA MKP10 2200P (2200PF 2.2nF 2,2nF) 1000V 5%
pitch:7.5mm Capacitor

★★★★★ Be the first to [write a review](#).



Seller : [electriclee](#) (13665) ★ [me](#) 99.8% Positive feedback

[Follow this seller](#) | [See other items](#) | Visit store: [World Famous Electronic Component](#)

Item condition: New

Quantity:

89 available / 11 sold

Price: US \$5.35



Doorknob Capacitor, High
Voltage Ceramic Capacitor
30kV 100pF
(151766918518)




Doorknob Capacitor, High
Voltage Ceramic Capacitor
15kV 5300pF
(361341199540)

Quantity: 6


AND THERE ARE SPECIFIC DETAILS ON HOW TO MAKE AND CONNECT THE COMPONENTS :



Resistor
1K 25W

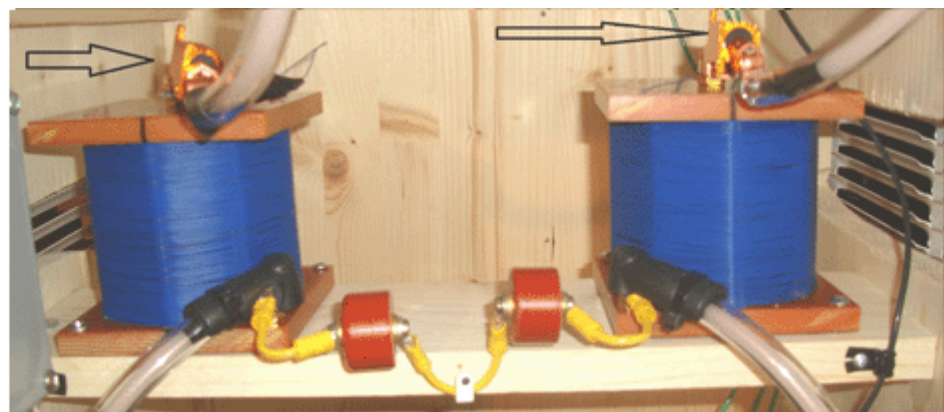


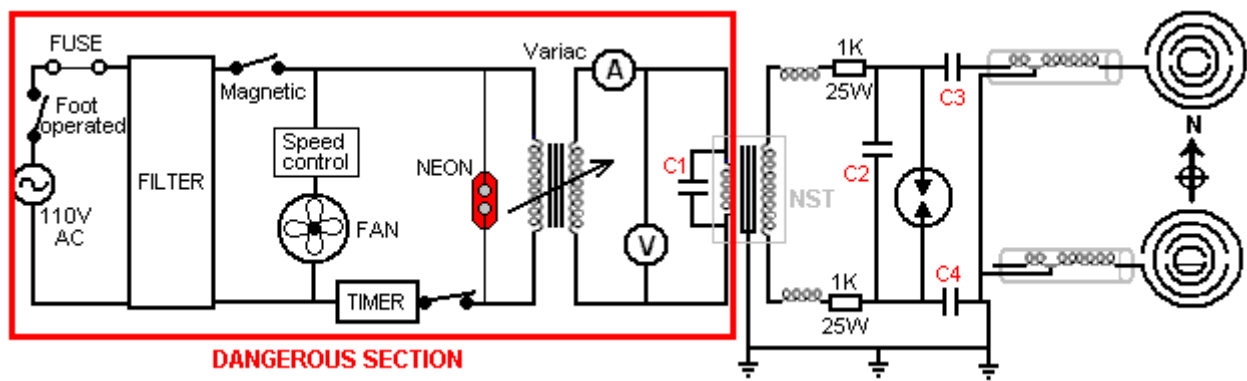HOWEVER, CARE NEEDS TO BE TAKEN WHEN WORKING WITH UNSHIELDED MAINS CONNECTIONS. FOR EXAMPLE :





THE SECTION OF THE CIRCUIT INSIDE THE RED RECTANGLE HAS DANGEROUS LOW-FREQUENCY HIGH VOLTAGES WHICH COULD KILL YOU IF YOU ARE CARELESS. CONSEQUENTLY, **LET ME STRESS THAT THIS PRESENTATION IS FOR INFORMATION PURPOSES ONLY AND MUST NOT BE CONSIDERED TO BE A RECOMMENDATION THAT YOU SHOULD ACTUALLY CONSTRUCT THIS DEVICE.**

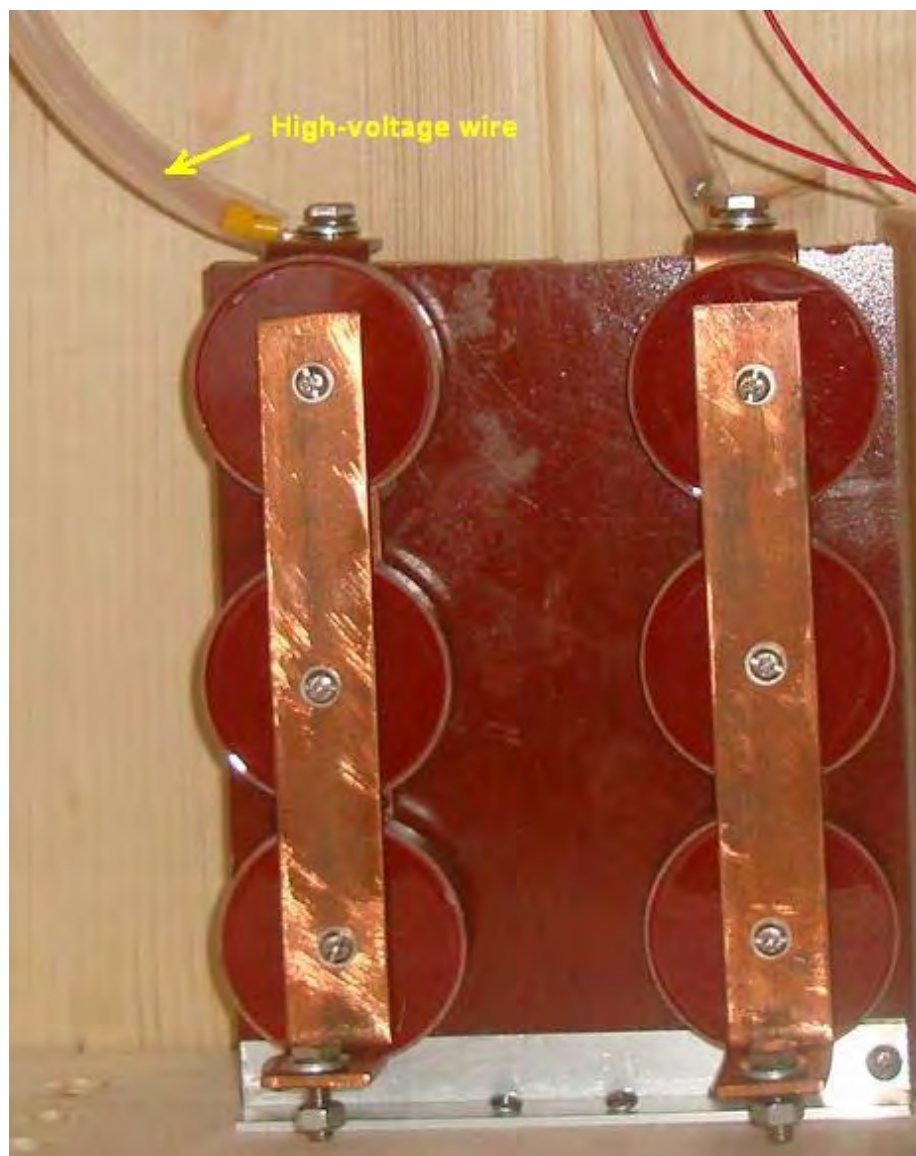THE HIGH VOLTAGE CAPACITORS ARE BUILT UP USING THE CAPACITORS SHOWN ABOVE. THEY ARE ASSEMBLED LIKE THIS :



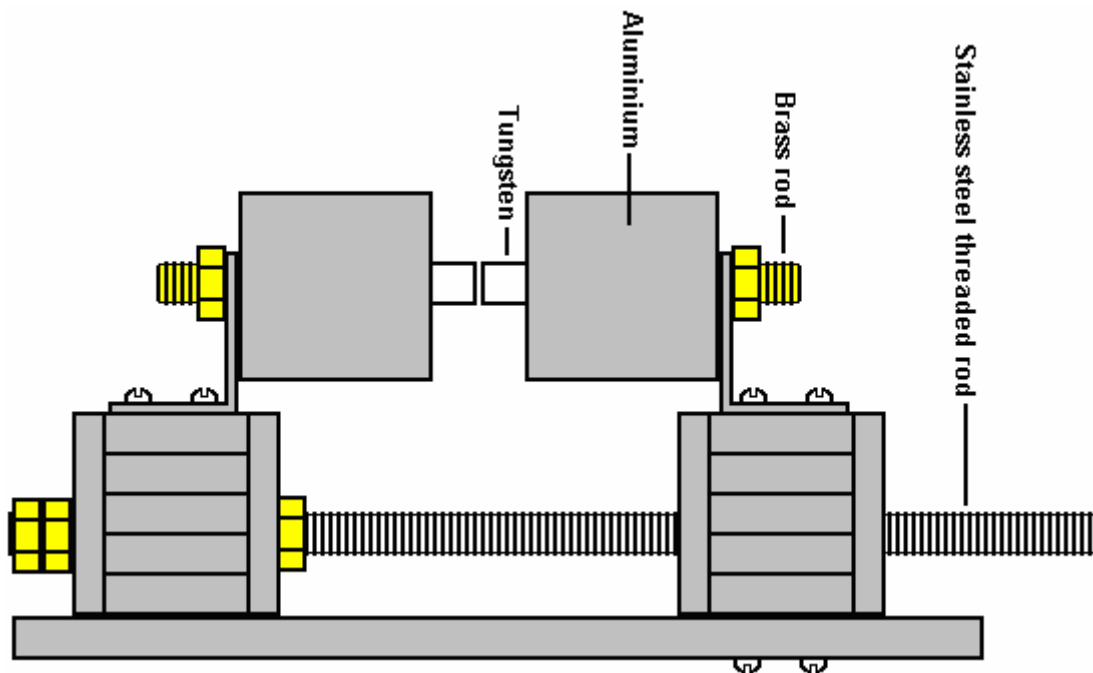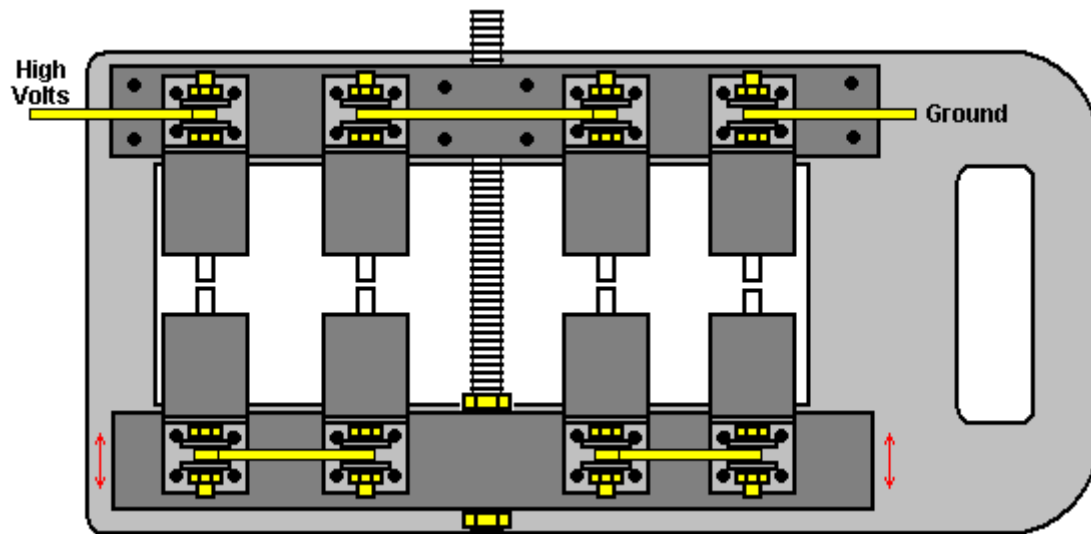ALSO, THE SPARK GAP IS CONSTRUCTED ON A UHMWP (Ultra High Molecular Weight Polythene) PLASTIC CHOPPING BOARD WHICH IS CUT TO THE REQUIRED SHAPE :



THIS STYLE OF CONSTRUCTION ALLOWS ALL OF THE SPARK GAPS TO BE ADJUSTED SIMULTANEOUSLY. THE ACTUAL SPARK GAPS ARE MADE FROM TUNGSTEN RODS EMBEDDED IN ALUMINIUM CYLINDERS :




1-1/2" Diameter 6061
Aluminum Round Rod 2"
Length T6511 Extruded 1.5
inch Dia
(322186173598)
Quantity: 10


THE COMPLETED UNIT LOOKS LIKE THIS :



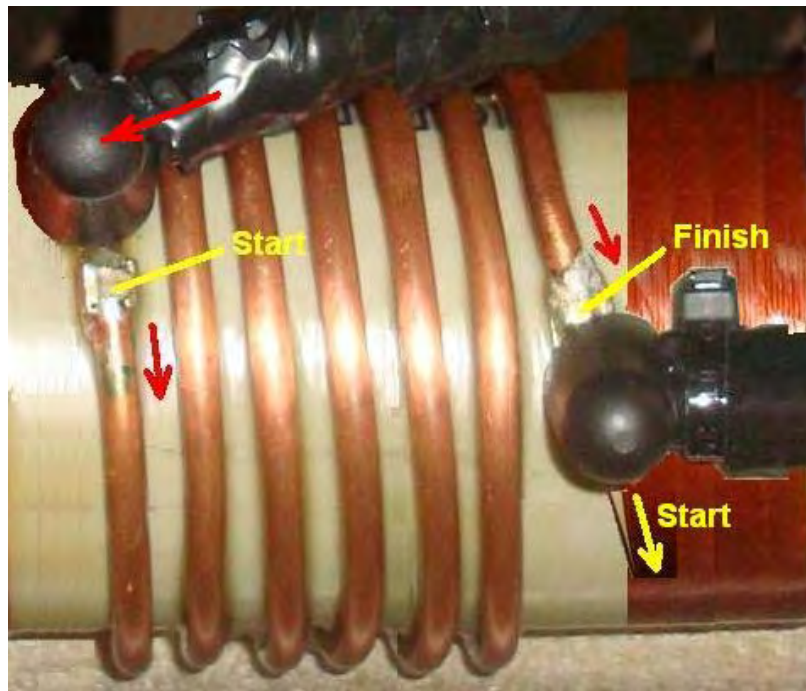THE COILS WHICH DRIVE THE ANTENNAS ARE MADE WITH TWO DIFFERENT WINDING MATERIALS, AND THEY ARE WOUND IN A CLOCKWISE DIRECTION :



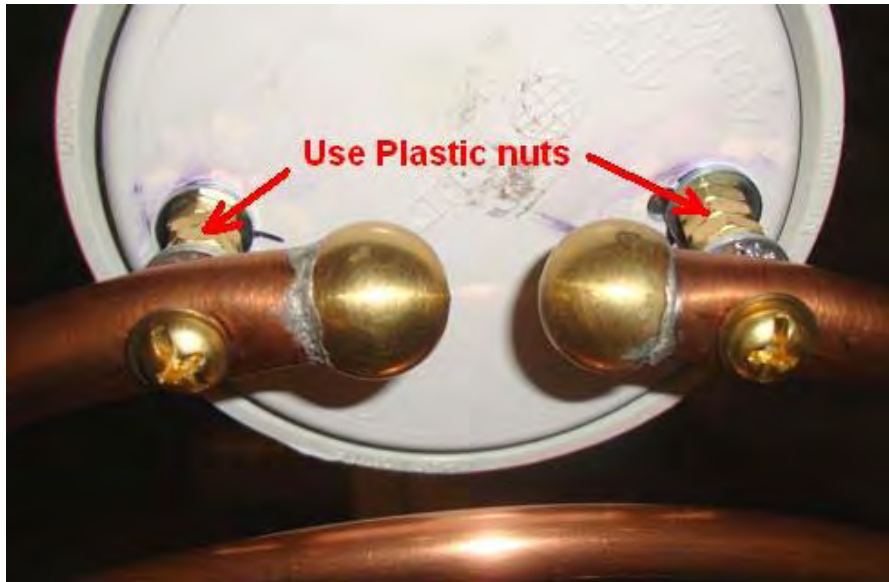
AND THE CONNECTIONS TO THE ANTENNA NEED TO BE PARTIALLY INSULATED TO AVOID SPARKING WHEN IN USE :




WHEN BEING USED, A WOODEN STOOL IS PLACED BETWEEN THE ANTENNAS :



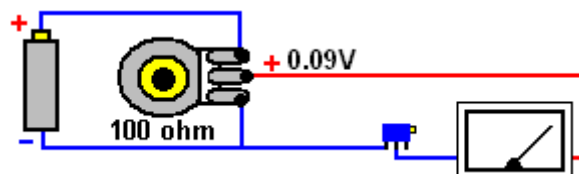
MOST TREATMENT SESSIONS ARE ABOUT 15 MINUTES LONG. HOWEVER, IT WOULD BE NICE TO KNOW THE LEVEL OF TRANSMISSION POWER BETWEEN THE AERIALS AND THAT CAN BE DETERMINED USING A SIMPLE METER. A PHILIPS TL6W/33 FLUORESCENT TUBE WHICH IS 220 mm (8.66 INCHES) LONG CAN BE USED FOR THIS. A 15-VOLT VOLTMETER IS SET UP TO SHOW FULL-SCALE DEFLECTION WHEN 0.09 VOLTS IS APPLIED TO IT:



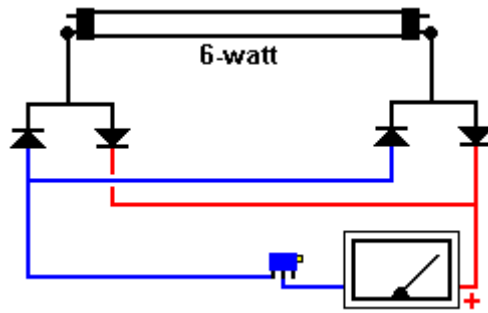AND WHEN THE 100 OHM PRESET IS SET CORRECTLY, THEN THE CIRCUIT IS COMPLETED LIKE THIS :



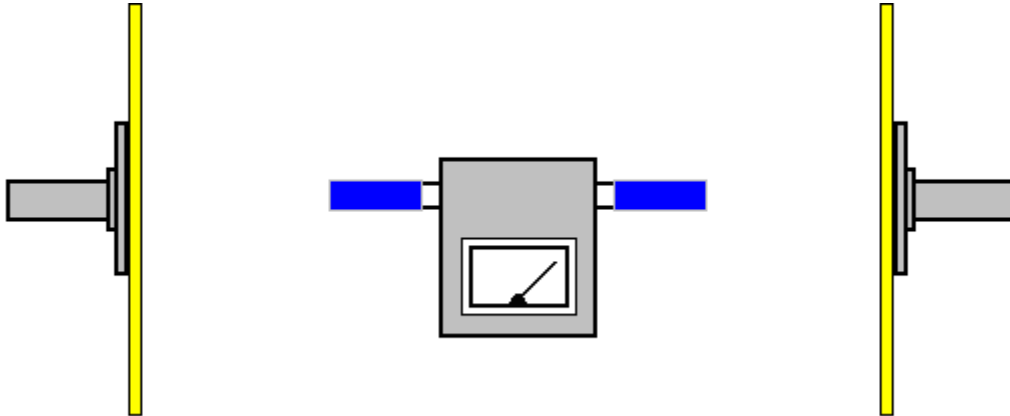AND THE UNIT CAN THEN BE PLACED ON THE CHAIR BETWEEN THE ANTENNAS AND THE WORKING VOLTAGE SET ON THE EQUIPMENT BEFORE TREATMENT IS COMMENCED :



THESE VERY BRIEF PRESENTATION NOTES CAN BE DOWNLOADED FROM THE FOLLOWING LINK: <http://www.free-energy-info.com/Health.pdf> BUT A VERY MUCH GREATER LEVEL OF DETAIL ON BUILDING AND USING THIS EQUIPMENT CAN BE FOUND IN THE FREE EBOOK: <http://www.free-energy-info.com/PJKbook.pdf>

VIDEO : <https://youtu.be/KS7TxVeYPng>